

DSP-CIS

Part-II : Filter Design & Implementation

Chapter-5 : Filter Realization

Marc Moonen

Dept. E.E./ESAT-STADIUS, KU Leuven

marc.moonen@kuleuven.be

www.esat.kuleuven.be/stadius/

Filter Design Process

- **Step-1 : Define filter specs**
Pass-band, stop-band, optimization criterion,...
- **Step-2 : Derive optimal transfer function**
FIR or IIR design **Chapter-4**
- **Step-3 : Filter realization** (block scheme/flow graph)
Direct form realizations, lattice realizations, ... **Chapter-5**
- **Step-4 : Filter implementation** (software/hardware)
Finite word-length issues, ... **Chapter-6**
Question: implemented filter = designed filter ?
'You can't always get what you want' -Jagger/Richards (?)

Chapter-5 : Filter Realization

- FIR Filter Realization
- IIR Filter Realization

PS: Will always assume *real-valued* filter coefficients

PS:

Q: Why bother
about many different
realizations for one and the
same filter?

A: See Chapter-6 !



FIR Filter Realization

FIR Filter Realization

=Construct (realize) LTI system (with delay elements, adders and multipliers), such that I/O behavior is given by..


$$y[k] = b_0 \cdot u[k] + b_1 \cdot u[k-1] + \dots + b_L \cdot u[k-L]$$

Several possibilities exist...

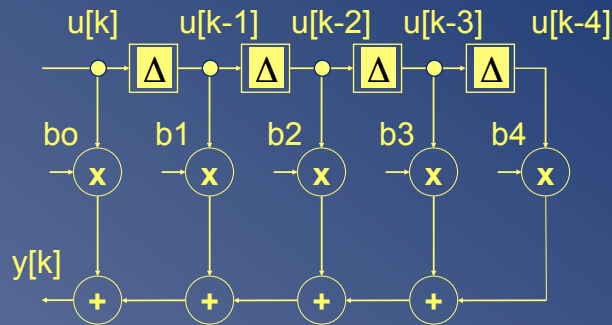1. Direct form
2. Transposed direct form
3. Lattice realization (LPC lattice)
4. Lossless lattice realization
5. Frequency-domain realization: see Part-IV


FIR / 1. Direct Form

$$y[k] = b_0 \cdot u[k] + b_1 \cdot u[k-1] + \dots + b_L \cdot u[k-L]$$




FIR / 2. Transposed Direct Form

Starting point is direct form :

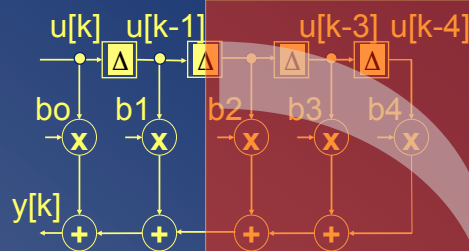


'Retiming' =

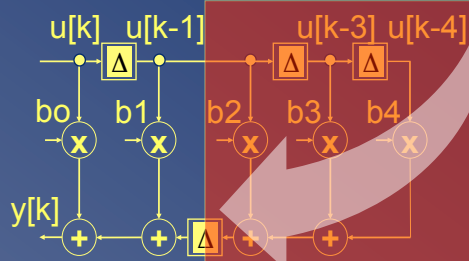- select subgraph (shaded)
- remove one delay element on all inbound arrows
- add one delay element on all outbound arrows



FIR / 2. Transposed Direct Form
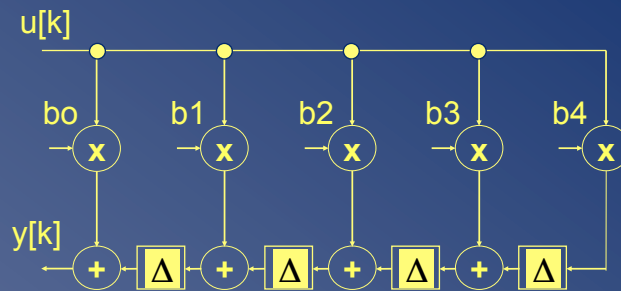
`Retiming' : repeated application results in...



i.e. `transposed direct form' (named after 'transposed' state space model)
 (=different software/hardware ('pipeline delays'), same i/o-behavior)

FIR / 3. Lattice Realization

Derived from combined realization of...

$$H(z): \quad y[k] = b_0 \cdot u[k] + b_1 \cdot u[k-1] + \dots + b_L \cdot u[k-L]$$

...with `flipped' version of $H(z)$

$$\tilde{H}(z) = z^{-L} \cdot H(z^{-1}): \quad \tilde{y}[k] = b_L \cdot u[k] + b_{L-1} \cdot u[k-1] + \dots + b_0 \cdot u[k-L]$$


Reversed (real-valued) coefficient vector results in...

$$\left| \tilde{H}(z) \right|_{z=e^{j\omega}}^2 = \tilde{H}(z) \cdot \tilde{H}(z^{-1}) \Big|_{z=e^{j\omega}} = \dots = \left| H(z) \right|_{z=e^{j\omega}}^2$$

- i.e. - same magnitude response
 - different phase response

FIR / 3. Lattice Realization

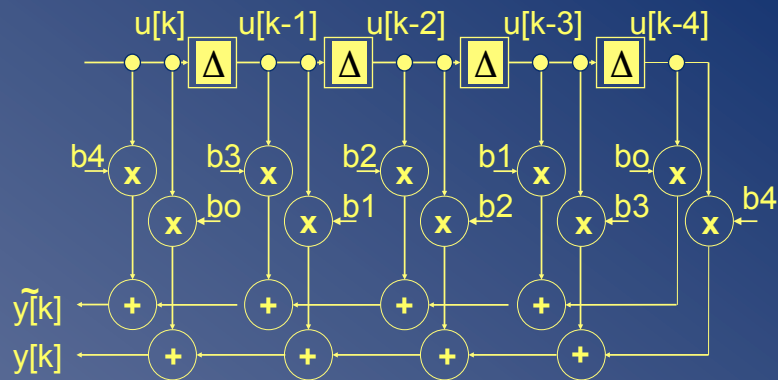Starting point is direct form realization...



Now 1 page of maths...

FIR / 3. Lattice Realization

$$\begin{bmatrix} \tilde{Y}(z) \\ Y(z) \end{bmatrix} = \begin{bmatrix} b_4 & b_3 & b_2 & b_1 & b_0 \\ b_0 & b_1 & b_2 & b_3 & b_4 \end{bmatrix} \cdot [1 \ z^{-1} \ \dots \ z^{-4}]^T \cdot U(z)$$

With $\kappa_0 = \frac{b_4}{b_0}$ if ($b_0 \neq 0$) and ($|\kappa_0| \neq 1$) this can be rewritten as

$$\begin{aligned} \begin{bmatrix} \tilde{Y}(z) \\ Y(z) \end{bmatrix} &= \begin{bmatrix} 1 & \kappa_0 \\ \kappa_0 & 1 \end{bmatrix} \begin{bmatrix} 0 & b'_3 & b'_2 & b'_1 & b'_0 \\ b'_0 & b'_1 & b'_2 & b'_3 & 0 \end{bmatrix} \cdot [1 \ z^{-1} \ \dots \ z^{-4}]^T \cdot U(z) \\ &= \begin{bmatrix} 1 & \kappa_0 \\ \kappa_0 & 1 \end{bmatrix} \begin{bmatrix} z^{-1} & 0 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} b'_3 & b'_2 & b'_1 & b'_0 \\ b'_0 & b'_1 & b'_2 & b'_3 \end{bmatrix} \cdot [1 \ z^{-1} \ \dots \ z^{-3}]^T \cdot U(z) \end{aligned}$$


order reduction

$$b'_0 = b_0, \quad b'_1 = \frac{b_1 - \kappa_0 b_3}{1 - \kappa_0^2}, \quad b'_2 = \frac{b_2 - \kappa_0 b_2}{1 - \kappa_0^2}, \quad b'_3 = \frac{b_3 - \kappa_0 b_1}{1 - \kappa_0^2}$$

PS: find fix for case $b_0=0$ PS: if $|\kappa_0|=1$, then transformation matrix $\begin{bmatrix} 1 & \kappa_0 \\ \kappa_0 & 1 \end{bmatrix}$ is rank-deficient

FIR / 3. Lattice Realization


This is equivalent to...

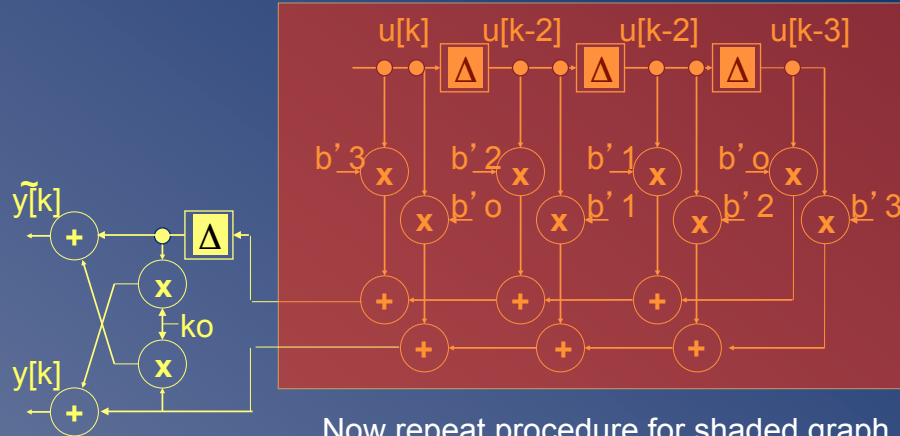

...Now repeat procedure for shaded graph
(=same structure as the one we started from)

FIR / 3. Lattice Realization

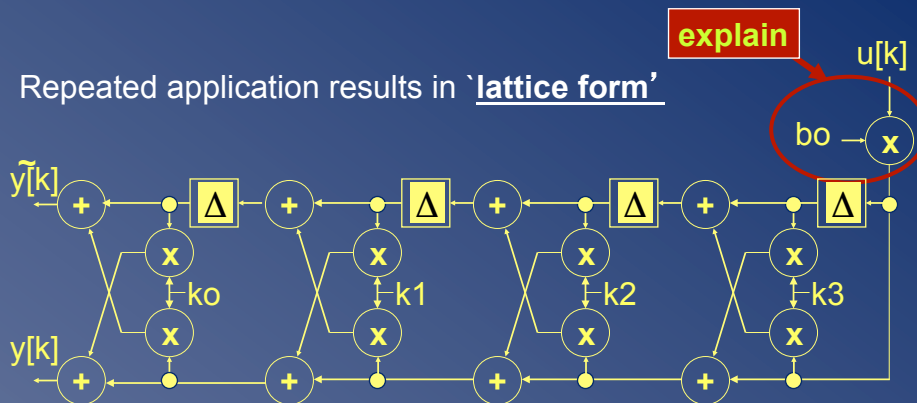Repeated application results in 'lattice form'



(= different software/hardware, same i/o-behavior)

FIR / 3. Lattice Realization

- Also known as 'linear predictive coding (LPC) lattice'
 K_i 's are so-called '**reflection coefficients**'
 Every set of b_i 's corresponds to a set of K_i 's, and vice versa
- Procedure for computing K_i 's from b_i 's corresponds to the well-known '**Schur-Cohn stability test**' (from control theory):
 Problem = for a given polynomial $B(z)$, how do we find out if all the zeros of $B(z)$ are 'stable' (i.e. lie inside unit circle) ?
 Solution = from b_i 's, compute reflection coefficients K_i 's (=procedure on previous slides). Zeros are (proved to be) stable iff all K_i 's satisfy $|K_i| < 1$!
- Procedure (page 10) breaks down if $|K_i|=1$ is encountered. Then have to select other realization (direct form, lossless lattice, ...) for $B(z)$
- Lattice form not overly relevant at this point, but sets stage for similar derivations that lead to more relevant realizations (read on...)

FIR / 4. Lossless Lattice Realization

Derived from combined realization of $H(z)$...

$$H(z): \quad y[k] = b_0.u[k] + b_1.u[k-1] + \dots + b_L.u[k-L]$$

...with

$$\tilde{H}(z): \quad \tilde{y}[k] = \tilde{b}_0.u[k] + \tilde{b}_1.u[k-1] + \dots + \tilde{b}_L.u[k-L]$$

...which is such that

$$H(z).H(z^{-1}) + \tilde{H}(z).\tilde{H}(z^{-1}) = 1 \quad (*)$$

PS : Interpretation ?... (see next slide)

PS : May have to scale $H(z)$ to achieve this (why?) (scaling omitted here)

FIR / 4. Lossless Lattice Realization

PS : Interpretation ?

When evaluated on the unit circle, formula (*) is equivalent to (for filters with real-valued coefficients)

$$|H(z)|_{z=e^{j\omega}}^2 + |\tilde{H}(z)|_{z=e^{j\omega}}^2 = 1$$

i.e. $H(z)$ and $\tilde{H}(z)$ are 'power complementary'
 (= form a 1-input/2-output 'lossless' system, see also below)

FIR / 4. Lossless Lattice Realization

PS : How is $\tilde{H}(z)$ computed ?

$$\tilde{H}(z) \cdot \tilde{H}(z^{-1}) = 1 - \underbrace{H(z) \cdot H(z^{-1})}_{R(z)}$$

Note that if z_i (and z_i^*) is a root of $R(z)$, then $1/z_i$ (and $1/z_i^*$) is also a root of $R(z)$. Hence can factorize $R(z)$ as...


$$\tilde{H}(z) \cdot \tilde{H}(z^{-1}) = \alpha^2 \prod_i (z^{-1} - z_i)(z - z_i) \rightarrow \tilde{H}(z) = \alpha \prod_i (z^{-1} - z_i)$$

Note that z_i 's can be selected such that all roots of $\tilde{H}(z)$ lie inside the unit circle, i.e. $\tilde{H}(z)$ is a minimum-phase FIR filter.

This is referred to as spectral factorization, $\tilde{H}(z)$ =spectral factor.

FIR / 4. Lossless Lattice Realization

This is equivalent to...

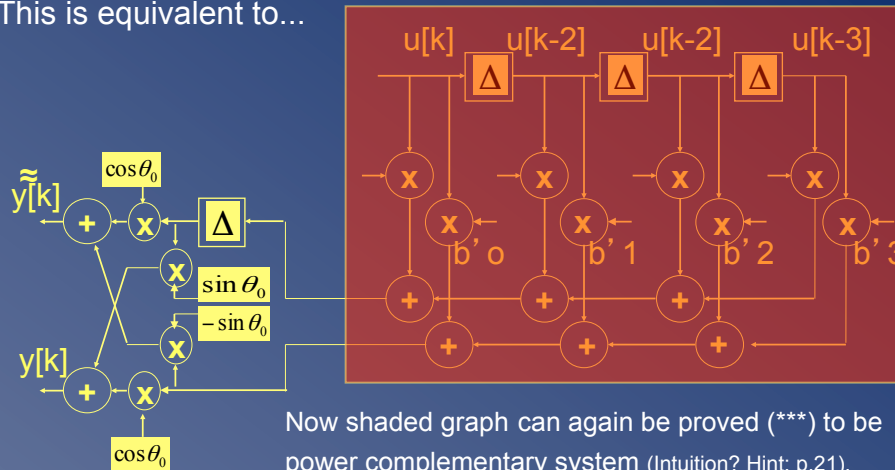


Now shaded graph can again be proved (***) to be power complementary system (Intuition? Hint: p.21). Hence can repeat procedure...

$$(***) \quad 1 - \begin{bmatrix} \hat{H}(z^{-1}) & H(z^{-1}) \\ \hat{H}(z) & H(z) \end{bmatrix} \begin{bmatrix} \hat{H}(z) \\ H(z) \end{bmatrix} = \begin{bmatrix} \hat{H}_\phi(z^{-1}) & H_\phi(z^{-1}) \\ \hat{H}_\phi(z) & H_\phi(z) \end{bmatrix} \begin{bmatrix} z & 0 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} \cos \theta_0 & \sin \theta_0 \\ -\sin \theta_0 & \cos \theta_0 \end{bmatrix} \begin{bmatrix} \cos \theta_0 & -\sin \theta_0 \\ \sin \theta_0 & \cos \theta_0 \end{bmatrix} \begin{bmatrix} z^{-1} & 0 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} \hat{H}_\phi(z) \\ H_\phi(z) \end{bmatrix} = \begin{bmatrix} \hat{H}_\phi(z^{-1}) & H_\phi(z^{-1}) \\ \hat{H}_\phi(z) & H_\phi(z) \end{bmatrix} \begin{bmatrix} \hat{H}_\phi(z) \\ H_\phi(z) \end{bmatrix}$$

FIR / 4. Lossless Lattice Realization

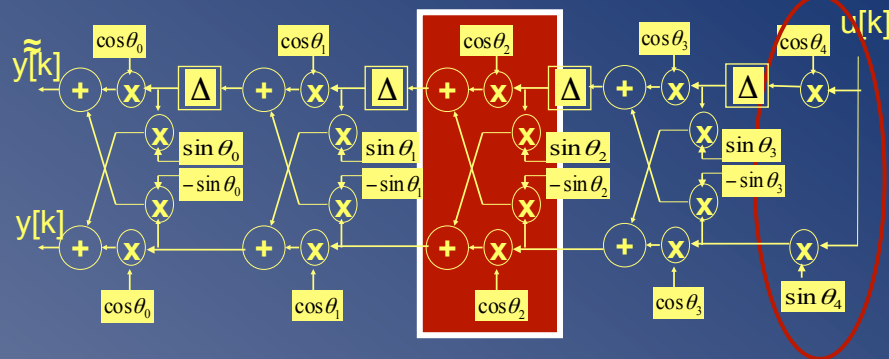Repeated application results in 'lossless lattice'



FIR / 4. Lossless Lattice Realization

Lossless lattice :


- Also known as 'paraunitary lattice'
- Each **2-input/2-output section** is based on an orthogonal transformation, which preserves norm/energy/power

$$\begin{bmatrix} OUT_1 \\ OUT_2 \end{bmatrix} = \begin{bmatrix} \cos \theta & -\sin \theta \\ \sin \theta & \cos \theta \end{bmatrix} \begin{bmatrix} IN_1 \\ IN_2 \end{bmatrix} \Rightarrow (IN_1)^2 + (IN_2)^2 = (OUT_1)^2 + (OUT_2)^2$$

i.e. forms a 2-input/2-output 'lossless' system (=time-domain view)
Overall system is realized as cascade of lossless sections (+delays), hence is itself also 'lossless' (see p.15, =freq-domain view)

FIR / 4. Lossless Lattice Realization

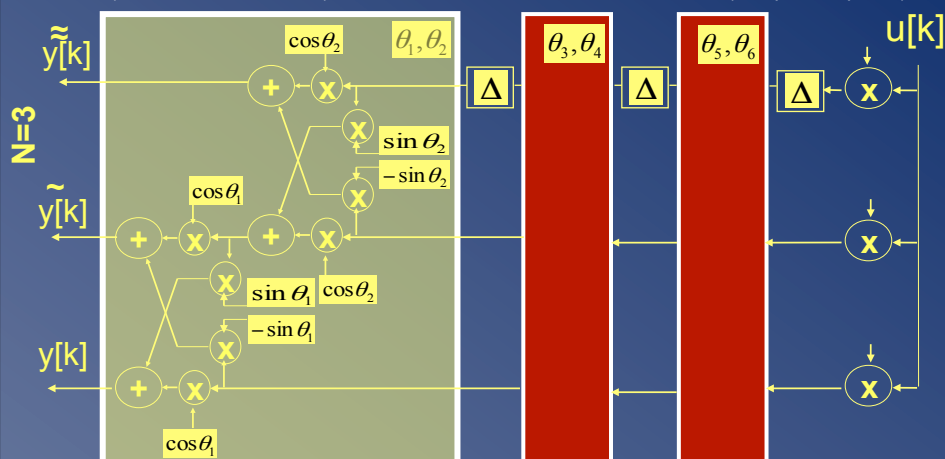PS : Can be generalized to 1-input N-output lossless systems
(will be used in Part-IV) (compare to p.20 !)



$$H(z)H(z^{-1}) + \tilde{H}(z)\tilde{H}(z^{-1}) + \tilde{\tilde{H}}(z)\tilde{\tilde{H}}(z^{-1}) = 1$$

explain/derive!

IIR Filter Realization

IIR Filter Realization

=Construct (realize) LTI system (with delay elements, adders and multipliers), such that I/O behavior is given by..


$$H(z) = \frac{B(z)}{A(z)} = \frac{b_0 + b_1z^{-1} + \dots + b_Lz^{-L}}{1 + a_1z^{-1} + \dots + a_Lz^{-L}}$$

Several possibilities exist...

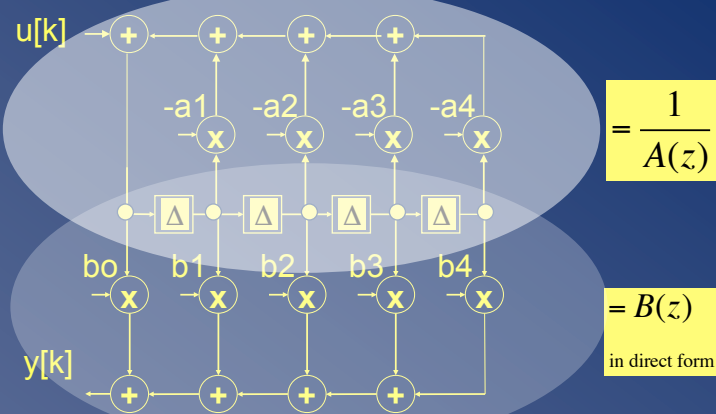1. Direct form
2. Transposed direct form
- PS: Parallel and cascade realization
4. Lattice-ladder realization
5. Lossless lattice realization

IIR / 1. Direct Form


$$H(z) = \frac{B(z)}{A(z)} = \frac{b_0 + b_1z^{-1} + \dots + b_Lz^{-L}}{1 + a_1z^{-1} + \dots + a_Lz^{-L}}$$



PS : If all $a_i=0$ (i.e. $H(z)$ is FIR), then this reduces to a direct form FIR

IIR / 2. Transposed Direct Form

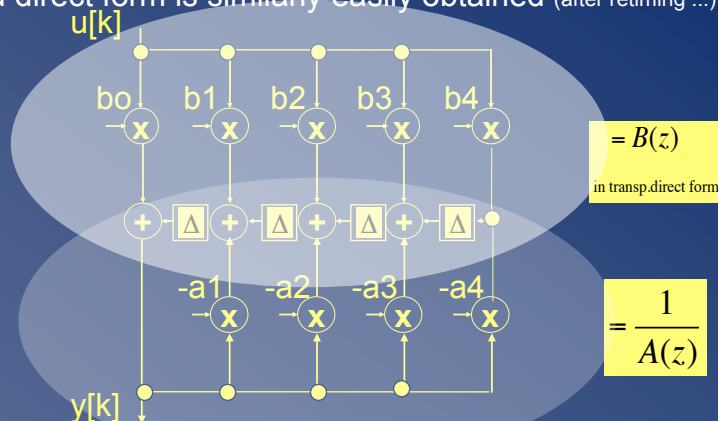Transposed direct form is similarly easily obtained (after retiming ...)



PS : If all $a_i=0$ (i.e. $H(z)$ is FIR), then this reduces to a transposed direct form FIR

IIR / PS: Parallel & Cascade Realization


- Parallel realization based on partial fraction decomposition

For simple poles

$$H(z) = \frac{B(z)}{A(z)} = c_0 + \sum_{i=1}^{L_1} \frac{\alpha_i}{1 + \beta_i z^{-1}} + \sum_{i=1}^{L_2} \frac{\gamma_i + \delta_i z^{-1}}{1 + \varepsilon_i z^{-1} + \varphi_N z^{-2}}$$

- Each term realized in, e.g., direct form
- Transmission zeros are realized iff signals from different sections exactly cancel out

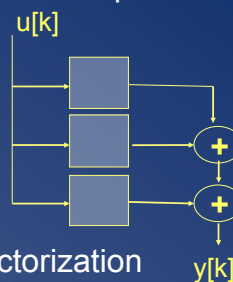(=difficult in finite word-length implementation)




- Cascade realization based on pole-zero factorization

For L even

$$H(z) = \frac{B(z)}{A(z)} = b_0 \cdot \prod_{i=1}^{L/2} \frac{1 + \alpha_i z^{-1} + \beta_i z^{-2}}{1 + \gamma_i z^{-1} + \delta_i z^{-2}}$$

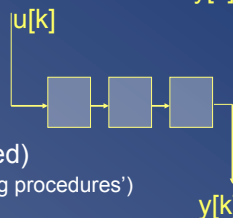- Each section ('biquad') realized in, e.g., direct form
- Cascade realization is not unique (details omitted)
(=multiple ways of pairing poles and zeros (need for 'pairing procedures') and multiple ways of ordering sections in cascade)



IIR / 3. Lattice-Ladder Realization

Derived from combined realization of

$$H(z) = \frac{B(z)}{A(z)} = \frac{b_0 + b_1 z^{-1} + \dots + b_L z^{-L}}{1 + a_1 z^{-1} + \dots + a_L z^{-L}}$$

with...


$$\tilde{H}(z) = \frac{\tilde{A}(z)}{A(z)} = \frac{a_L + a_{L-1} z^{-1} + \dots + 1 \cdot z^{-L}}{1 + a_1 z^{-1} + \dots + a_L z^{-L}}$$

- Numerator polynomial is denominator polynomial with reversed coefficient vector (see also p.8)
- Hence $\tilde{H}(z)$ is an 'all-pass' (= 'SISO lossless') filter :

$$\tilde{H}(z) \cdot \tilde{H}(z^{-1}) = 1 \quad \left| \tilde{H}(z) \right|_{z=e^{j\omega}}^2 = \frac{\left| \tilde{A}(z) \right|_{z=e^{j\omega}}^2}{\left| A(z) \right|_{z=e^{j\omega}}^2} = 1$$

IIR / 3. Lattice-Ladder Realization

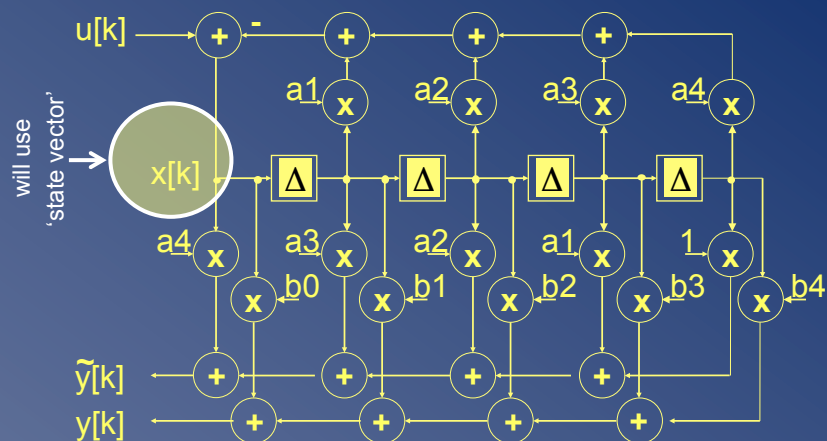Starting point is direct form realization...



IIR / 3. Lattice-Ladder Realization

$$\begin{bmatrix} U(z) \\ \tilde{Y}(z) \\ Y(z) \end{bmatrix} = \begin{bmatrix} 1 & a_1 & a_2 & a_3 & a_4 \\ a_1 & a_3 & a_2 & a_1 & 1 \\ b_1 & b_3 & b_2 & b_1 & 1 \end{bmatrix} \begin{bmatrix} 1 \\ z^{-1} \\ z^{-2} \\ z^{-3} \\ z^{-4} \end{bmatrix} X(z)$$

$$\begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & -b_1 & 1 \end{bmatrix} \begin{bmatrix} U(z) \\ \tilde{Y}(z) \\ Y(z) \end{bmatrix} = \begin{bmatrix} 1 & a_1 & a_2 & a_3 & a_4 \\ a_1 & a_3 & a_2 & a_1 & 1 \\ b'_1 & b'_3 & b'_2 & b'_1 & 0 \end{bmatrix} \begin{bmatrix} 1 \\ z^{-1} \\ z^{-2} \\ z^{-3} \\ z^{-4} \end{bmatrix} X(z)$$

with $b'_1 = b_1 - b_4 a_4$, $b'_3 = b_3 - b_4 a_3$, $b'_2 = b_2 - b_4 a_2$, $b'_1 = b_1 - b_4 a_1$

Now proceed as on page 11 (FIR lattice)

$\kappa_0 = \frac{a_1}{a_0} = \frac{a_1}{1}$ ($\theta = 1 \neq 0$) if $|a_1| \neq 1$ (see also next page):

$$\begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & -b_1 & 1 \end{bmatrix} \begin{bmatrix} U(z) \\ \tilde{Y}(z) \\ Y(z) \end{bmatrix} = \begin{bmatrix} 1 & \kappa_0 & 0 \\ \kappa_0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & a'_1 & a'_2 & a'_3 & 0 \\ 0 & a'_3 & a'_2 & a'_1 & 1 \\ b'_1 & b'_3 & b'_2 & b'_1 & 0 \end{bmatrix} \begin{bmatrix} 1 \\ z^{-1} \\ z^{-2} \\ z^{-3} \\ z^{-4} \end{bmatrix} X(z)$$

$$\begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & -b_1 & 1 \end{bmatrix} \begin{bmatrix} U(z) \\ \tilde{Y}(z) \\ Y(z) \end{bmatrix} = \begin{bmatrix} 1 & \kappa_0 & 0 \\ \kappa_0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & a'_1 & a'_2 & a'_3 \\ 0 & a'_3 & a'_2 & a'_1 & 1 \\ b'_1 & b'_3 & b'_2 & b'_1 & 0 \end{bmatrix} \begin{bmatrix} 1 \\ z^{-1} \\ z^{-2} \\ z^{-3} \\ z^{-4} \end{bmatrix} X(z)$$

$a'_0 = a_0 = 1$, $a'_1 = \frac{a_1 - a_4 a_4}{1 - a_4^2}$, $a'_2 = \frac{a_2 - a_4 a_3}{1 - a_4^2}$, $a'_3 = \frac{a_3 - a_4 a_2}{1 - a_4^2}$

If $A(z) =$ stable polynomial (should be!),
Then $|K_0| < 1$ (cfr. Shur-Cohn). Hence define

$$\sin \theta_0 = \kappa_0, \quad \cos \theta_0 = \sqrt{1 - (\kappa_0)^2} \quad (\neq 0)$$

$$\begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & -b_1 & 1 \end{bmatrix} \begin{bmatrix} U(z) \\ \tilde{Y}(z) \\ Y(z) \end{bmatrix} = \begin{bmatrix} 1 & \sin \theta_0 & 0 \\ \sin \theta_0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 & 0 \\ 0 & z^{-1} & 0 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & a'_1 & a'_2 & a'_3 \\ 0 & a'_3 & a'_2 & a'_1 & 1 \\ b'_1 & b'_3 & b'_2 & b'_1 & 0 \end{bmatrix} \begin{bmatrix} 1 \\ z^{-1} \\ z^{-2} \\ z^{-3} \\ z^{-4} \end{bmatrix} X(z)$$


$$\begin{bmatrix} 1 & \sin \theta_0 & 0 \\ \sin \theta_0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 & 0 \\ 0 & z^{-1} & 0 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & a'_1 & a'_2 & a'_3 \\ 0 & a'_3 & a'_2 & a'_1 & 1 \\ b'_1 & b'_3 & b'_2 & b'_1 & 0 \end{bmatrix} \begin{bmatrix} 1 \\ z^{-1} \\ z^{-2} \\ z^{-3} \\ z^{-4} \end{bmatrix} X(z) = \begin{bmatrix} U_0(z) \\ \tilde{Y}_0(z) \\ Y_0(z) \end{bmatrix}$$

Rearrange the first 2 rows

$$\begin{bmatrix} U(z) \\ \tilde{Y}(z) \end{bmatrix} = \begin{bmatrix} 1 & \sin \theta_0 \\ \sin \theta_0 & 1 \\ \cos \theta_0 & \cos \theta_0 \end{bmatrix} \begin{bmatrix} U_0(z) \\ \tilde{Y}_0(z) \\ z^{-1} \tilde{Y}_0(z) \end{bmatrix} \text{ into } \begin{bmatrix} U_0(z) \\ \tilde{Y}_0(z) \end{bmatrix} = \begin{bmatrix} \cos \theta_0 & -\sin \theta_0 \\ \sin \theta_0 & \cos \theta_0 \end{bmatrix} \begin{bmatrix} U(z) \\ z^{-1} \tilde{Y}(z) \end{bmatrix}$$


IIR / 3. Lattice-Ladder Realization

Then this is equivalent to...

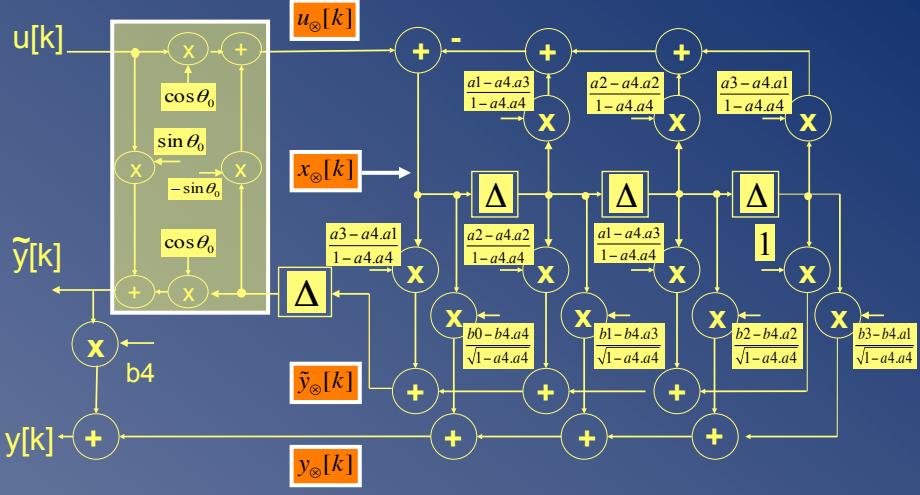


IIR / 3. Lattice-Ladder Realization

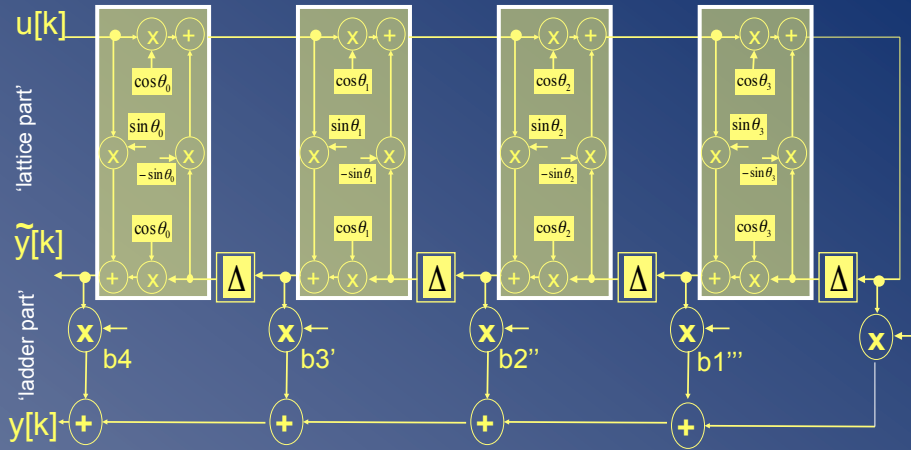Procedure can be repeated (explain), leads to 'lattice-ladder form'



IIR / 3. Lattice-Ladder Realization

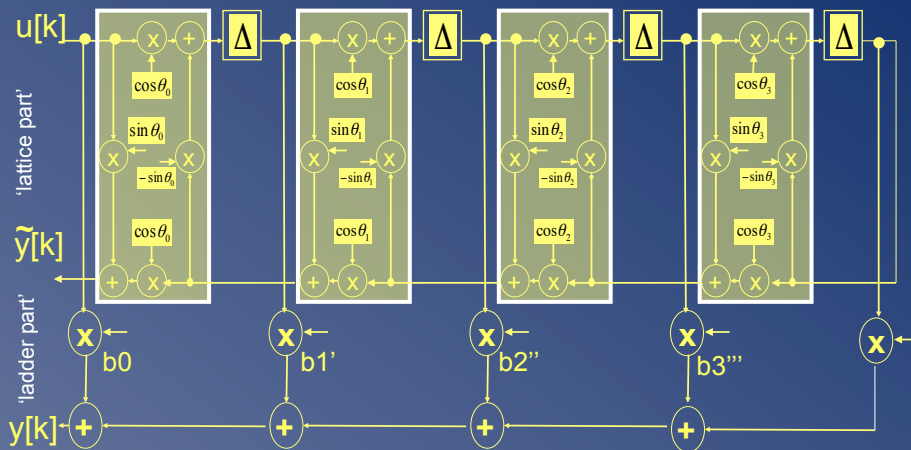PS: Similar derivation leads to 2nd 'lattice-ladder' form



IIR / 3. Lattice-Ladder Realization

- K_i 's (=sin(theta_i) !) are 'reflection coefficients'
- Procedure for computing K_i 's from a_i 's again corresponds to 'Schur-Cohn' stability test
- Orthogonal transformations correspond to 2-input/2-output 'lossless' sections (=time-domain view).


$$\begin{bmatrix} OUT_1 \\ OUT_2 \end{bmatrix} = \begin{bmatrix} \cos \theta & \sin \theta \\ -\sin \theta & \cos \theta \end{bmatrix} \begin{bmatrix} IN_1 \\ IN_2 \end{bmatrix} \Rightarrow (IN_1)^2 + (IN_2)^2 = (OUT_1)^2 + (OUT_2)^2$$

Cascade of lossless sections (+delays) is also 'lossless',
i.e. 'all-pass' (see p.27, =freq-domain view)

IIR / 3. Lattice-Ladder Realization

PS : Note that the all-pass part corresponds to $A(z)$ (i.e. L angles θ_i correspond to L coeffs a_i) while the ladder part corresponds to $B(z)$. If all $a_i=0$ (i.e. $H(z)$ is FIR), then all $\theta_i=0$, hence the all-pass part reduces to a delay line, and the lattice-ladder form reduces to a direct-form FIR.

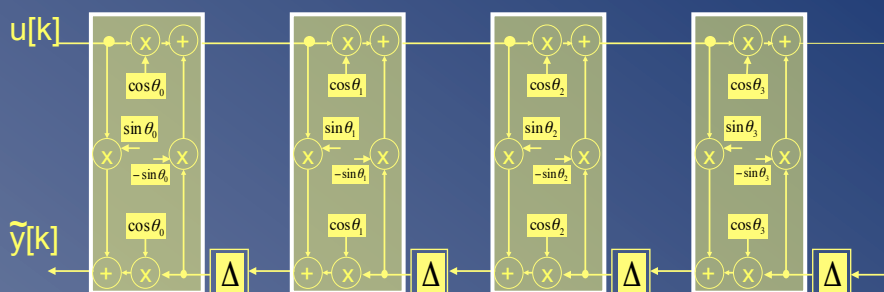PS : 'All-pass' part (SISO $u[k] \rightarrow \tilde{y}[k]$) is known as 'Gray-Markel' structure



IIR / 4. Lossless Lattice Realization

Derived from combined realization of (possibly rescaled, as on p.14)

$$H(z) = \frac{B(z)}{A(z)} = \frac{b_0 + b_1 z^{-1} + \dots + b_L z^{-L}}{1 + a_1 z^{-1} + \dots + a_L z^{-L}}$$

with...
$$\tilde{H}(z) = \frac{\tilde{B}(z)}{A(z)} = \frac{\tilde{b}_0 + \tilde{b}_1 z^{-1} + \dots + \tilde{b}_L z^{-L}}{1 + a_1 z^{-1} + \dots + a_L z^{-L}}$$

such that...


$$H(z) \cdot H(z^{-1}) + \tilde{H}(z) \cdot \tilde{H}(z^{-1}) = 1 \quad (**)$$

$$\Rightarrow B(z) \cdot B(z^{-1}) + \tilde{B}(z) \cdot \tilde{B}(z^{-1}) = A(z) \cdot A(z^{-1})$$

i.e. $\tilde{H}(z)$ and $H(z)$ are 'power complementary' (p.15)

IIR / 4. Lossless Lattice Realization

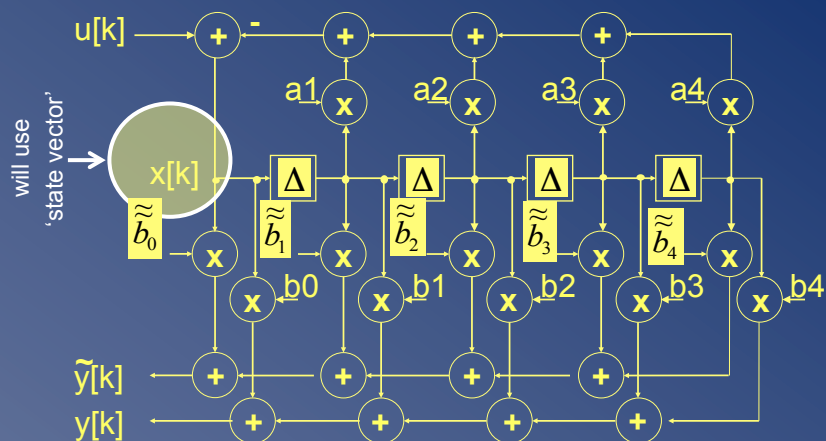Starting point is direct form realization...



IIR / 4. Lossless Lattice Realization

$$\begin{bmatrix} U(z) \\ \tilde{Y}(z) \\ Y(z) \end{bmatrix} = \begin{bmatrix} a_0 & a_1 & a_2 & a_3 & a_4 \\ \tilde{b}_0 & \tilde{b}_1 & \tilde{b}_2 & \tilde{b}_3 & \tilde{b}_4 \\ b_0 & b_1 & b_2 & b_3 & b_4 \end{bmatrix} \begin{bmatrix} 1 \\ z^{-1} \\ \dots \\ z^{-4} \end{bmatrix} X(z)$$

$$\begin{bmatrix} 1 & 0 & 0 \\ 0 & \cos \psi_0 & -\sin \psi_0 \\ 0 & \sin \psi_0 & \cos \psi_0 \end{bmatrix} \begin{bmatrix} a_0 & a_1 & a_2 & a_3 & a_4 \\ \tilde{b}_0 & \tilde{b}_1 & \tilde{b}_2 & \tilde{b}_3 & \tilde{b}_4 \\ b_0 & b_1 & b_2 & b_3 & b_4 \end{bmatrix} \begin{bmatrix} 1 \\ z^{-1} \\ \dots \\ z^{-4} \end{bmatrix} X(z)$$

for $\frac{\sin \psi_0}{\cos \psi_0} = \frac{b_1}{b_0}$ and $\tilde{b}_1 = \sqrt{(\tilde{b}_0)^2 + (b_1)^2}$

$$\begin{bmatrix} 1 & 0 & 0 \\ 0 & \cos \psi_0 & -\sin \psi_0 \\ 0 & \sin \psi_0 & \cos \psi_0 \end{bmatrix} \begin{bmatrix} 1 & \sin \theta_0 & 0 \\ \cos \theta_0 & \cos \theta_0 & 0 \\ \sin \theta_0 & 1 & 0 \end{bmatrix} \begin{bmatrix} a'_0 & a'_1 & a'_2 & a'_3 & a'_4 \\ \tilde{b}'_0 & \tilde{b}'_1 & \tilde{b}'_2 & \tilde{b}'_3 & \tilde{b}'_4 \\ b'_0 & b'_1 & b'_2 & b'_3 & b'_4 \end{bmatrix} \begin{bmatrix} 1 \\ z^{-1} \\ \dots \\ z^{-4} \end{bmatrix} X(z)$$

for $\sin \theta_0 = \frac{a_1}{b'_0}$ (o) and $\tilde{b}'_1 = \dots = \sqrt{(\tilde{b}'_0)^2 + (b'_1)^2 - (a_1)^2}$

PS: right-hand side of (o) has modulus < 1 (hence $|\sin \theta_0| \neq 1$, $\cos \theta_0 \neq 0$) which follows from 'modulus property' for (**): p.35:

if (**): for $H(z) = \tilde{H}(z)$ non-constant (i.e. order ≥ 1) and $\tilde{H}(z)$ stable then:

$$|H(z=0)|^2 + |\tilde{H}(z=0)|^2 > 1 \Rightarrow \frac{(\tilde{b}_0)^2 + (b_0)^2}{(\tilde{b}_0)^2 + (b_0)^2} > 1$$

Now it is proved that $\tilde{b}''_0 = 0$

From (**): p.35 it follows that

$$b_0 b_4 + \tilde{b}_0 \tilde{b}_4 = a_0 a_4 \Rightarrow \begin{bmatrix} a_0 & \tilde{b}_0 & b_0 \\ -1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} a_4 \\ \tilde{b}_4 \\ b_4 \end{bmatrix} = 0$$

$\Rightarrow \dots$ plug in transformation with θ_0 and $\psi_0 \dots$

$$\Rightarrow \begin{bmatrix} a'_0 & \tilde{b}'_0 & b'_0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} a'_4 \\ \tilde{b}'_4 \\ b'_4 \end{bmatrix} = 0$$


$\tilde{b}''_0 = 0$ (cfr. $\tilde{b}''_4 \neq 0$)

order reduction

$$\begin{bmatrix} U(z) \\ \tilde{Y}(z) \\ Y(z) \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 \\ 0 & \cos \psi_0 & -\sin \psi_0 \\ 0 & \sin \psi_0 & \cos \psi_0 \end{bmatrix} \begin{bmatrix} 1 & \sin \theta_0 & 0 \\ \cos \theta_0 & \cos \theta_0 & 0 \\ \sin \theta_0 & 1 & 0 \end{bmatrix} \begin{bmatrix} a'_0 & a'_1 & a'_2 & a'_3 \\ \tilde{b}'_0 & \tilde{b}'_1 & \tilde{b}'_2 & \tilde{b}'_3 \\ b'_0 & b'_1 & b'_2 & b'_3 \end{bmatrix} \begin{bmatrix} 1 \\ z^{-1} \\ \dots \\ z^{-3} \end{bmatrix} X(z)$$

IIR / 4. Lossless Lattice Realization

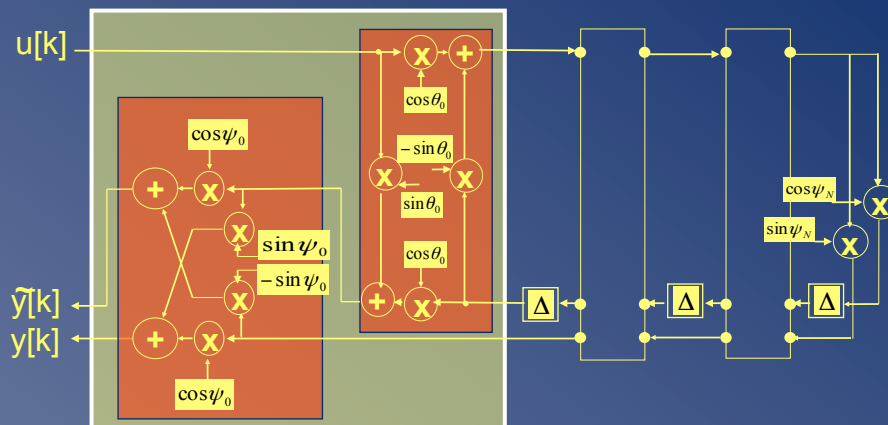Rearranging rows, etc., and repeating the order-reduction process, leads to...



IIR / 4. Lossless Lattice Realization

- Orthogonal transformations correspond to (3-input 3-output) 'lossless sections'

$$\begin{bmatrix} OUT_1 \\ OUT_2 \\ OUT_3 \end{bmatrix} = \begin{bmatrix} \cdot & \cdot & \cdot \\ \cdot & \cdot & \cdot \\ \cdot & \cdot & \cdot \end{bmatrix} \begin{bmatrix} IN_1 \\ IN_2 \\ IN_3 \end{bmatrix}$$

$$\Rightarrow (IN_1)^2 + (IN_2)^2 + (IN_3)^2 = (OUT_1)^2 + (OUT_2)^2 + (OUT_3)^2$$

Overall system is realized as cascade of lossless sections (+delays), hence is itself also 'lossless'

- PS : If all $a_i=0$ (i.e. $H(z)$ is FIR), then all $\theta_i=0$ and then this reduces to FIR lossless lattice !
- PS : If all $\phi_i=0$, then this reduces to Gray-Markel structure !

IIR / 4. Lossless Lattice Realization

- PS : Can be generalized to 1-input N-output lossless systems
(=combine p.22 & p.38 !)

